



MURANG'A UNIVERSITY COLLEGE

(A Constituent College of Jomo Kenyatta University of Agriculture and Technology)

DEPARTMENT: ELECTRICAL ENGINEERING

LEVEL: DIPLOMA

CLASS: MRUC/EE/P/14DJ

TERM/SEMESTER: I1 YEAR 11

ACADEMIC YEAR: 2014/2015

UNIT: MEASUREMENT AND FAULT DIAGNOSIS

UNIT CODE: SEE1212

DATE: 17TH APRIL 2015

TIME: 2 HOURS

Instructions to candidates

This paper contains two sections A and B

Answer question one (COMPULSORY) and any other two question in section B.

You should have the following for this examination;

- Drawing instruments
- Scientific calculator

SECTION A (COMPULSORY)

Qn. 1(a) State the three fundamental quantities which mechanical quantities can be expressed in

(3marks)

(b) Derive the dimensions of the following mechanical quantities

(i) Velocity

(3marks)

(ii) Acceleration

(3marks)

(iii) Force

(3marks)

(c) The dimensional formula for potential difference is $(U^{1/2}M^{1/2}L^{3/2}T^{-2})$. Show how the formula is derived

(6marks)

(d) The expression of eddy current loss P per meter length of a wire may be written as

$$P \propto f^a B_m^b d^c \rho^g$$

Where f-frequency

B_m -maximum flux density

d-diameter of the wire

ρ -resistivity of wire mate

and a; b; c and g are constants, determine the values of a; b; c and g from the dimensions of quantities involved. Length (L), Mass (M), Time (T) and current (I) may be taken as fundamental quantities. Derive the dimensions of each quantity from fundamentals.

N.B. Do not reproduce the dimension from the memory

(12mrks)

SECTION B (Answer any two questions)

Qn. 2.(a) With the aid of a diagram explain the working multi-range ammeter
(10mrks)

(b) Design a multi-range d.c milli-ammeter using a basic movement with an internal resistance $R_m = 60 \Omega$ and a full scale deflection current of $I_m = 1\text{mA}$. The range required is 0-10mA, 0-50mA, 0-100mA, and 0-500mA. (10mrks)

Qn. 3. (a) With the aid of a circuit diagram derive the general equation of an A.C. Bridge

(10mrks)

(b) A bridge consist of the following

Arm ab-a choke coil having a resistance R_1 and inductance L_1

Arm bc-a non-inductive resistance R_3

Arm cd-a mica condenser C_4 in series with non-inductive resistance R_4

Arm da-a non-inductive resistance R_2

When this bridge is fed from a source of 800HZ balance is obtained under following conditions

$R_2 = 2520 \Omega$, $R_3 = 760 \Omega$, $C_4 = 0.45 \mu\text{F}$, $R_4 = 65.4 \Omega$. The series resistance of capacitor is 0.5Ω . Calculate the resistance and inductance of the choke coil. The supply is connected between a and c and the detector is between b and d (10mrks)

Qn.4. With the aid of a diagram describe the working of a cathode ray oscilloscope

(20mrks)