



# MURANG'A UNIVERSITY OF TECHNOLOGY

## SCHOOL OF ENGINEERING & TECHNOLOGY

DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING

UNIVERSITY POSTGRADUATE EXAMINATION

2018/2019 ACADEMIC YEAR

**FIRST YEAR SECOND SEMESTER EXAMINATION FOR MASTER OF TECHNOLOGY**

EET 623 – ADVANCED POWER SYSTEMS PROTECTION

DURATION: 3 HOURS

DATE: 14/5/19

TIME: 2-5 P.M.

**Instructions to candidates:**

1. Answer **Any Four** questions.
2. Mobile phones are not allowed in the examination room.
3. You are not allowed to write on this examination question paper.

## QUESTION ONE

(a) An alternator rated at 10kv protected by the balanced circulating current system has its neutral grounded through a resistance of 10ohms. The protective relay is set to operate when there is an out-of-balance current of 1.8A in the pilot wires, which are connected to secondary windings of 1000/5 ratio current transformers. Determine the:

- i. The percentage winding which remains unprotected. (4marks)
- ii. The maximum value of the earthing resistance required to protect 80% of the winding. (4marks)


(b) The line-to-ground voltages on the high voltage side of a step- up transformer are 100kV, 33kV and 38kV on phase a, b and c respectively. The voltage of phase 'a' leads that of phase 'b' by  $100^\circ$  and lags that of phase 'c' by  $176.5^\circ$ . Determine analytically the symmetrical components of voltage. (6marks)

(c) Show that for a simulation of a solidly grounded, unloaded alternator under line-to-ground fault, all the three sequence networks are required and must be connected in series. (10marks)

(d) A small generating station has a bus bar divided into three sections. Each section is connected to a tie-bar with reactors each rated at 5MVA and 0.1p.u reactance. A generator of 8MVA rating and 0.15p.u reactance is connected to each section of the busbar. Determine the short-circuit capacity of the breaker if a 3-phase fault takes place on one of the sections of the bus bar. (6marks)

## QUESTION TWO

Figure Q2 shows a sample power system network:

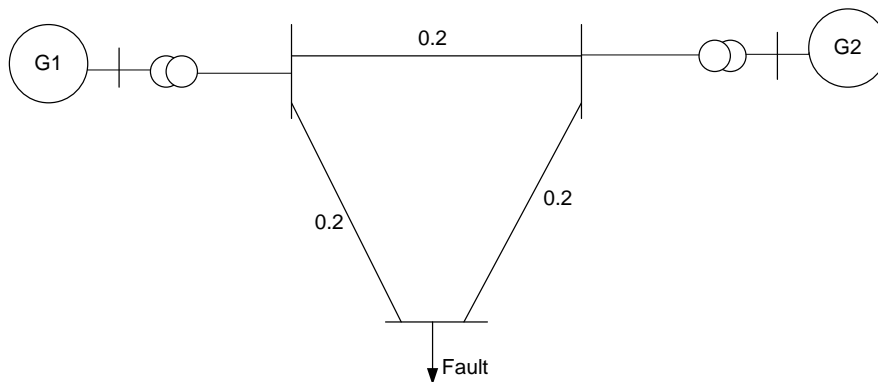

- a) Draw the thevenin passive network for this system (4marks)
- b) Develop the  $Z_{bus}$  matrix. (8marks)
- c) For a solid three phase fault current,  $V_{1f}$  and  $V_{2f}$  and fault current in line 1-2. (8marks)

### **QUESTION THREE**

A 50MVA, 11kV, synchronous generator has sub-transient reactance of 20%. The generator supplies two motors over a transmission line with transformers at both ends as shown in fig Q3. The motors have rated inputs of 30 and 15MVA, both 10kV, with 25% sub-transient reactance. The three-phase transformers are both rated 60MVA, 10.8/121 kV, with leakage reactance of 10% each. Assume zero sequence reactance for the generator and motors of 6% each. Current limiting reactors of 2.5 ohms each are connected in the neutral of the generator and motor N<sub>o</sub> 2.

The zero sequence reactance of the transmission line is 300 ohms. The series reactance of the line is 100 ohms. Draw the:

- Positive sequence network. (8marks)
- Negative sequence network. (6marks)
- Zero sequence network. (6marks)

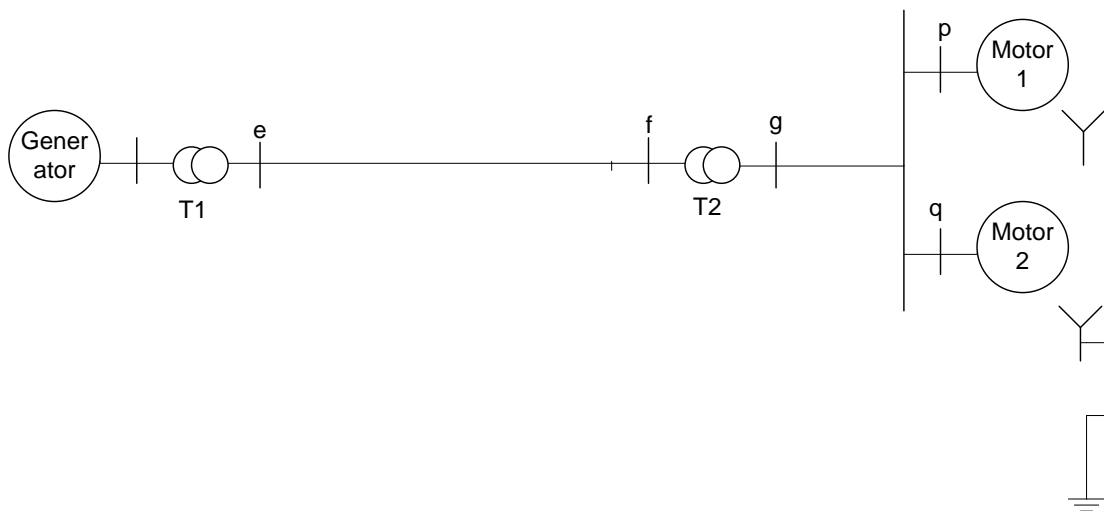


Fig Q3

### **QUESTION FOUR**

A 30MVA, 13.2 kV synchronous generator has a solidly grounded neutral. The positive, negative and zero sequence impedances are 0.30, 0.40 and 0.05pu respectively. Determine the following:

- The value of reactance that must be placed in the generator neutral so that the fault current for a line-to-ground fault of zero fault impedance shall not exceed the rated line current. (3marks)
- The value of the resistance in the neutral that will serve the same purpose as in (a) above. (3marks)
- The value of reactance that must be placed in the neutral of the generator to restrict the fault current to the ground to rated line current for a double line to ground fault. (6marks)
- Determine the magnitude of the line currents when the ground current is restricted as in (c) above. (5marks)
- As the reactance in the neutral is indefinitely increased, determine the values of limiting line currents. (3marks)

### **QUESTION FIVE**

- a) Explain the essential qualities of a protective system. (5marks)
- b) Explain with the aid of sketches the four tripping characteristics of a relay. (6marks)
- c) Considering the power system network shown in fig Q5,
- Determine the direction of flow of power between bus 1 and bus 2. (3marks)
  - Locate the position of load impedance onto the R-jX plane. (3marks)
  - Calculate the maximum load ability of a distance relay with mho characteristics for zone3 (3marks)

