



MURANG'A UNIVERSITY OF TECHNOLOGY

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ENGINEERING AND TECHNOLOGY

TVET EXAMINATION

2023/2024 ACADEMIC YEAR

**SECOND YEAR FIRST SEMESTER EXAMINATION FOR DIPLOMA IN
ELECTRIC AND ELECTRONICS ENGINEERING
&
INFORMATION TECHNOLOGY**

IT/OS/ICT/CC/01 – BASIC ELECTRONICS

DURATION: 3 HOURS

INSTRUCTIONS TO CANDIDATES:

1. Answer ALL questions
2. Mobile phones are not allowed in the examination room.
3. You are not allowed to write on this examination question paper.

SECTION A (30 MARKS)

ATTEMPT ALL QUESTIONS IN THIS SECTION


Q1. Define the following laws in Electronics (6 marks)

- a) Kirchoffs current law
- b) Kirchoffs voltage law
- c) Ohms law and state the symbol for ohms

Q2. An electric heater consumes 1.8 mJ when connected to a 250V supply for 30 minutes. Find the power rating of the heater and the current taken from the supply (5 marks)

Q3. A battery of emf 12V supplies a current of 5A for 2 minutes. How much energy is supplied in this time (4 marks)

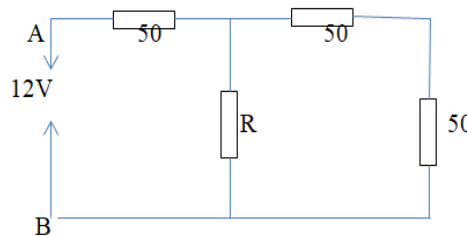Q4. What is the value of the unknown resistor R in the figure below if the voltage drop across the 500Ω resistor is 2.5 volts




all the values are in ohms. Determine the current across all the resistors I_{50} , I_{50} , I_R , I_{500} (10 marks)

Q5. A mass of 500kg is raised to a height of 6m in 30s. Find (5 marks)

- a) The work done
- b) The power developed

SECTION B (20 MARKS)

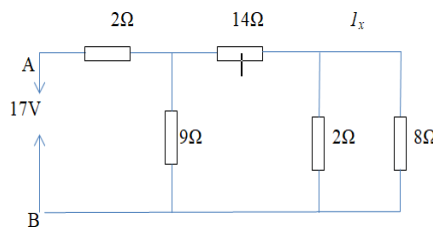Q6. a) For the arrangement below find the equivalent resistance R_{eq} and calculate the value of current I_x (7 marks)



b) Define the term capacitance and state the applications of a capacitor. (3 marks)

c) For how long must a charging current of 2A be fed to a capacitor to raise the p.d. between its plate by 500V. (3 marks)

d) Proof that the equivalent resistance of a series connected circuit is $R_1 + R_2 + R_3 \dots \dots R_n = R_{eq}$ using the loop impedance of a circuit. (7 marks)