



## MURANG'A UNIVERSITY COLLEGE

( A Constituent College of Jomo Kenyatta University of Agriculture and Technology)

**SCHOOL:** ENGINEERING AND TECHNOLOGY

**DEPARTMENT:** MECHANICAL ENGINEERING

**LEVEL:** DIPLOMA

**CLASS:** MRUC/ME/P/14DS

**SEMESTER:** II YEAR1

**JAN-APRIL 2015**

**ACADEMIC YEAR:** 2014/2015

**EXAM : MAIN**

**UNIT:** ELECTRICAL ENGINEERING SCIENCE

**UNIT CODE:** P1102

**DATE:** 29/04 APRIL 2015

**TIME:** 3 HOURS

### *Instructions to candidates*

This exam paper contains section `A` and `B` with five questions in total

Answer Question one (1) and any other two


You should have the following for this examination;

- Drawing instruments
- Scientific calculator
- No mobile phones allowed in the exam

### **SECTION `A` COMPULSORY**

- Q.1**
- a) Briefly explain the difference between metallic and covalent bonding (4 marks)
- b) State Ohms law (2 marks)
- c) Define the following terms as applied in electrical quantities
- I. Volt.
  - II. Ohm.
  - III. Potential difference. (6 marks)
- d) Determine the total resistance and the terminal voltage for the network shown in Figure 1, below (8 marks)

Fig 1

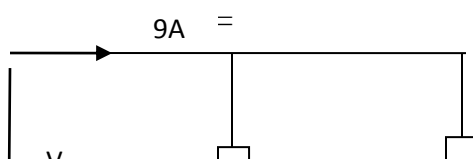

e) Explain first Faradays law as applied in electrolysis. (3 marks)

f) Briefly explain the concept of force on a single straight current carrying conductors (4 marks)

g) Explain the difference between magnetic circuit and electrical circuit. (3 marks)

**SECTION B ANSWER ANY TWO QUESTION IN THIS SECTION**

**Q.2** a) State any four factors that affects the resistance of a conductor (4 marks)

b) With the aid of a diagram show that the total equivalent resistance of 'n' series connected resistors is given by


$$R_S = R_1 + R_2 + R_3 + \dots + R_n \quad (5 \text{ marks})$$

c) A series circuit containing three resistors  $R_1$ ,  $R_2$ , and  $R_3$  dissipates 20 mW when connected to 30 V supply. Calculate the p.d. across  $R_1$  given that  $R_2$  dissipates 10mW and the resistance of  $R_3$  is  $3K\Omega$  (7 marks)

d) A micro computer system takes a current of 2.5A at a supply of 10v/ Calculate the daily energy consumption if it operates at 12 hours per day (4 marks)

**Q.3** a) i) State Kirchhoff's law (4 marks)

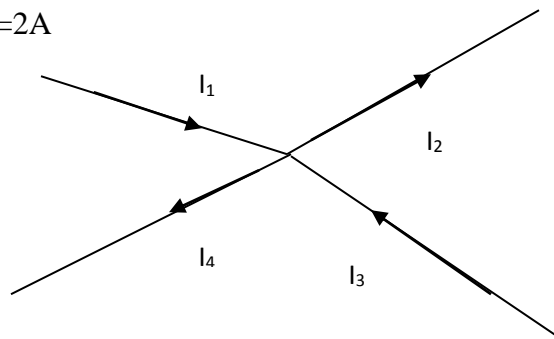ii) For the network junction shown in the figure 2 below, calculate current  $I_3$  given that  $i_1=3A$   $I_2=-4A$  and  $i_4=2A$  (4 marks)




b) Explain the following types of circuit connections

- I. Parallel
- II. Series- Parallel (4marks)

c) Fig 3 below shows a series -parallel network. Using Kirchhoff's laws calculate

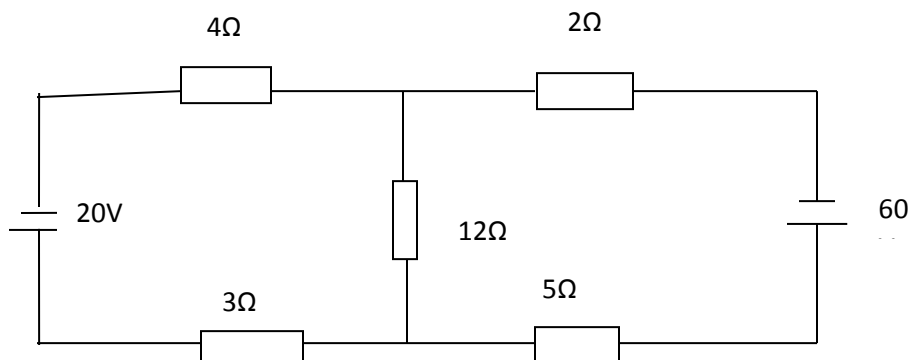- I. Current through each branch
- II. P.d. across the  $12\Omega$  resistor
- III. Energy absorbed by the  $12\Omega$  resistor in 40 min. (8 marks)



**Q.4a)** Define the following terms as used in batteries

- a) Polarization
- b) Local action (4 marks)

b) State

- (i) Difference between primary and secondary cells.
- (ii) Indication of a fully charged lead acid cell. (4marks)
- (c) With the aid of a circuit diagram, explain the method of constant

Voltage, battery charging (6marks)

d) A battery of 60 cell is charged from a supply of 230V. Each cell has an e.m.f. of 2 volts at the start of charge and 2.4V at the end. If internal resistance of each cell is  $0.1\Omega$ , determine for a load of  $19\Omega$  connected in the circuit.

- (i) Initial Charging current
- (ii) Final charging current (4 marks)

**Q5** (a) Define the following terms with reference to magnetism.

- I. Relative permeability.
- II. Magneto motive force (4 marks)

b) With the aid of a labeled diagram, describe a simple hysteresis loop (8 marks)

c) A steel ring has a round cross sectional area of  $5\text{cm}^2$ . If the mean flux length of the magnetic circuit is  $50\text{cm}$ , find the magneto motive force required to produce a flux of  $500\ \mu\text{Wb}$  in the iron. Take magnetic field strength of mild steel  $=950\ \text{A/M}$

(8 marks)