



MURANG'A UNIVERSITY COLLEGE
(A Constituent College of Jomo Kenyatta University of Agriculture and Technology)

DEPARTMENT: ELECTRICAL AND ELECTRONIC ENGINEERING
DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING
MAIN EXAMINATION

CLASS: MRUC/EEP/14DM
LEVEL: DIPLOMA
SEMESTER: 1
ACADEMIC YEAR: 2014/15
YEAR OF STUDY: 2
UNIT: ANALOGUE ELECTRONICS II
UNIT CODE: SEE1202
DATE: 24TH APRIL 2013 **TIME: 2 HOURS**

Instructions to candidates

This paper contains four **4** Questions

Attempt question **one (1)** and any **other two (2)** questions

You should have the following for this examination;

- Drawing instruments
- Scientific calculator

➤ **NO MOBILE PHONES ARE ALLOWED WITHIN THE EXAMINATION ROOM!!!!!!**

Question 1 (30 marks)

- a). Explain why it is desirable to mid-point bias class A amplifier [2mks]
- b). State the primary disadvantage of using an amplifier with swamping resistor [3mks]
- c). Explain the cause of crossover distortion in a class B transistor amplifier [2mks]
- d). Show that the maximum theoretical efficiency for a class A amplifier is 25%. [4mks]
- e). Explain what determine the class of operation of an amplifier. [2mks]
- f). Explain why is class C operation more efficient than class A operation in transistor amplifier circuits. [2mks]
- g). List the two operating states of the class D amplifier? [2mks]
- h). State the purpose of amplifier coupling network? [2mks]
- i). With the aid of diagrams, explain the operation of a turned class C amplifier [6mks]
- j). List four characteristics of an ideal operational amplifier. [3mks]
- k). Name the type of current that flows through n-channel JFET? [1mrks]

Question 2 (20 marks)

- a). State the bias conditions that must exist for a transistor to operate as an amplifier [2mks]
- b). Determine the following DC values for the amplifier in figure 1
 $V_B, V_E, I_E, I_C, V_C,$ and V_{CE} [6mks]
- c). Determine the following AC values for the amplifier in figure 1
 $R_{in(base)}, R_{in}, A_v, A_i, A_p$ [10mks]

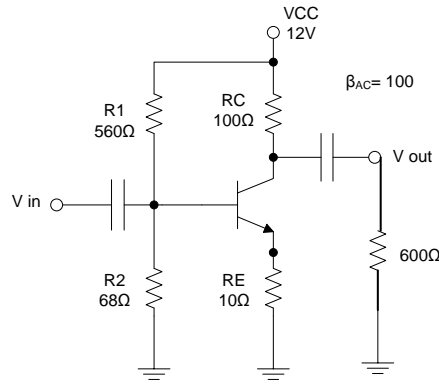


Figure 1

- d). plot the AC load line [2mks]

Question 3 (20 marks)

- a). Name two factors that determine the voltage gain of a CE amplifier [2mks]
- b). State two operating states of the class D amplifier? [2mks]
- c). A certain FET common source (CS) amplifier has g_m of $2600\mu S$, R_L of $22k\Omega$ and R_D of $12k\Omega$. $v_{gs}=v_{in}=40mV$. Determine the voltage gain and v_{out} for both load and unloaded amplifier. [8mks]
- d). Describe how changes in V_{GS} are related to changes in I_D for a n-channel JFET amplifier [2mks]
- e). In the circuit figure 2, let $R_1=5k\Omega$, $R_f=20k\Omega$ and $v_i=1V$. A load resistor of $5k\Omega$ is connected at the output. Calculate [6mks]
- i) Output voltage, V_o
 - ii) Closed loop gain, A_{CL}
 - iii) The load current, i_L

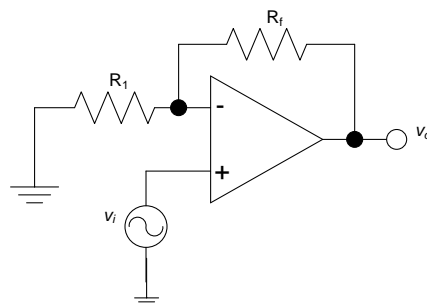


Figure 2

Question 4 (20mrks)

- a). Explain why class C amplifiers unsuitable for voice and music amplification? **3mks**
- b). List three advantages of class C amplifiers **3mks**
- c). For the circuit of figure 3, determine bandwidth (BW), $i_{c(sat)}$, power dissipated by the transistor P_{Dif} if $v_{ce(sat)}=0.2V$, Maximum power load P_L , tank circuit power P_{tank} , maximum source power P_{DC} , and the efficiency. **14mks**

