



**MURANG'A UNIVERSITY COLLEGE**  
(A constituent College of Jomo Kenyatta University of Agriculture and Technology)

**SPH 2172 (PHYSICS) MAIN EXAM**

**DATE: 17 DECEMBER 213**


**TIME: 2 HOURS**

---

Answer Question **One** And Any Other **Two** Questions


**QUESTION 1**

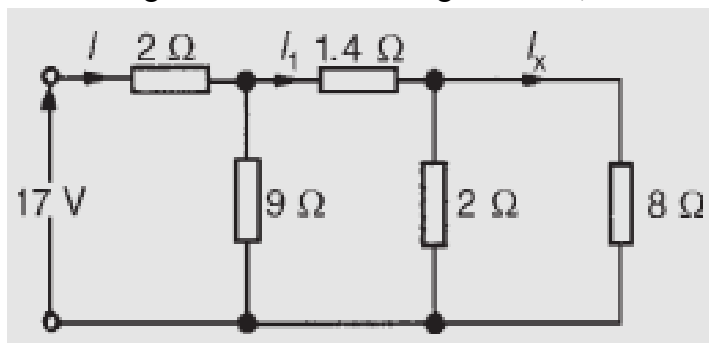- a) State Kirchoff's laws. [2mks]
- b) You are given three resistors  $R_1=10\Omega$ ,  $R_2=20\Omega$  and  $R_3=30\Omega$ . You are also given a 240V
- c) source of emf. Draw a circuit diagram showing how you will connect these resistors so as
- d) to obtain minimum effective resistance. Find also the supply current and the current flowing through the  $R_2$ . [5mks]
- e) For the arrangement shown in the figure below, find the current  $I_x$ . [4mks]



- f) Find the equivalent resistance of three resistors of resistance  $R_1$ ,  $R_2$  and  $R_3$  when connected in series. [4mks]
- g) A magnetizing force of 8000A/m is applied to a circular magnetic circuit of mean diameter 30 cm by passing a current through a coil wound on the circuit. If the coil is uniformly wound around the circuit and has 750 turns, find the current in the coil. [4mks]

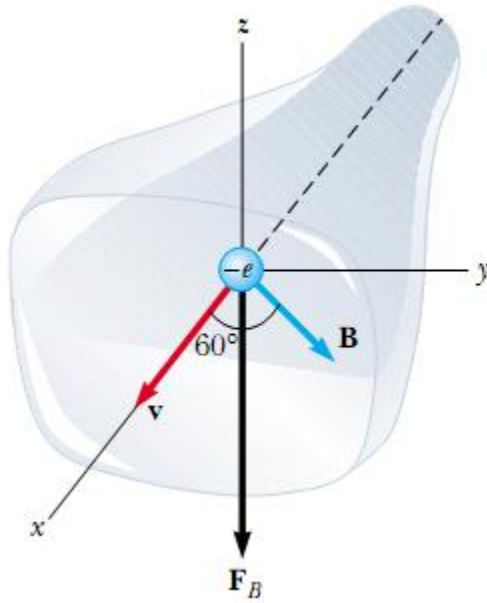- h) An electron in a television picture tube moves toward the front of the tube with a speed of  $8.0 \times 10^6$  m/s along the x axis as shown below. Surrounding the neck of the tube are coils of wire that create a magnetic field of magnitude 0.025 T, directed at an angle of  $60^\circ$  to the x axis and lying in the xy plane. Find the magnitude of the magnetic force. [4mks]



- i) A cell has an internal resistance of  $0.02\Omega$  and an e.m.f. of 2.0V. Calculate its terminal p.d. if it delivers 5A. [3mks]
- j) The resistance of a coil of aluminium wire at  $18^\circ\text{C}$  is  $200\Omega$ . The temperature of the wire is increased and the resistance rises to  $240\Omega$ . If the temperature coefficient of resistance of aluminium is  $0.0039/^\circ\text{C}$  at  $18^\circ\text{C}$ , determine the temperature to which the coil has risen. [4mks]

## QUESTION 2

- a) Determine the resistance of 1200m of copper cable having a diameter of 12mm if the resistivity of copper is  $1.7 \times 10^{-8} \Omega\text{m}$ . [ 4mks]
- b) Determine the colour coding for a  $47 \text{ k}\Omega$  having a tolerance of  $\pm 5\%$ . The table below can be used. [ 3mks]

Colour	Significant Figures	Multiplier	Tolerance
Silver	–	$10^{-2}$	$\pm 10\%$
Gold	–	$10^{-1}$	$\pm 5\%$
Black	0	1	–
Brown	1	10	$\pm 1\%$
Red	2	$10^2$	$\pm 2\%$
Orange	3	$10^3$	–
Yellow	4	$10^4$	–
Green	5	$10^5$	$\pm 0.5\%$
Blue	6	$10^6$	$\pm 0.25\%$
Violet	7	$10^7$	$\pm 0.1\%$
Grey	8	$10^8$	–
White	9	$10^9$	–
None	–	–	$\pm 20\%$

- c) Determine the value of a resistor marked as 4M7M using the table below. Tolerance is indicated as follows: F =  $\pm 1\%$ , G =  $\pm 2\%$ , J =  $\pm 5\%$ , K =  $\pm 10\%$  and M =  $\pm 20\%$  3mks

Resistance Value	Marked as:
0.47 $\Omega$	R47
1 $\Omega$	1R0
4.7 $\Omega$	4R7
47 $\Omega$	47R
100 $\Omega$	100R
1 k $\Omega$	1K0
10 k $\Omega$	10K
10 M $\Omega$	10M


- d) A d.c. electric motor consumes 36MJ when connected to a 250V supply for 1 hour. Find the power rating of the motor and the current taken from the supply. [4mks]
- e) Define conductance and state its units. [2mks]
- f) A conductor has a conductance of  $50\mu\text{S}$ . What is its resistance? Find the p.d across the conductor if a current of 0.5A is flowing through it. [4mks]

### QUESTION 3

- a) Calculate the resistance per unit length of a 22-gauge nichrome wire, which has a radius of 0.321 mm. The resistivity of nichrome is  $1.5 \times 10^{-6} \Omega\text{m}$ . [4mks]
- b) A resistance thermometer, which measures temperature by measuring the change in resistance of a conductor, is made from platinum and has a resistance of  $50 \Omega$  at  $20^\circ\text{C}$ . When immersed in a vessel containing melting indium, its resistance increases to  $76.8 \Omega$ . Calculate the melting point of the indium. Take the temperature coefficient of platinum  $\alpha = 3.92 \times 10^{-3} \text{ }^\circ\text{C}^{-1}$ . (5mks)
- c) Define the emf of a battery. [1mk]
- d) A battery has an emf of 12.0 V and an internal resistance of  $0.05 \Omega$ . Its terminals are connected to a load resistance of  $3 \Omega$ .
- Find the current in the circuit and the terminal voltage of the battery. [4mks]
  - Calculate the power delivered to the load resistor, the power delivered to the internal resistance of the battery, and the power delivered by the battery. [6mks]

### QUESTION 4

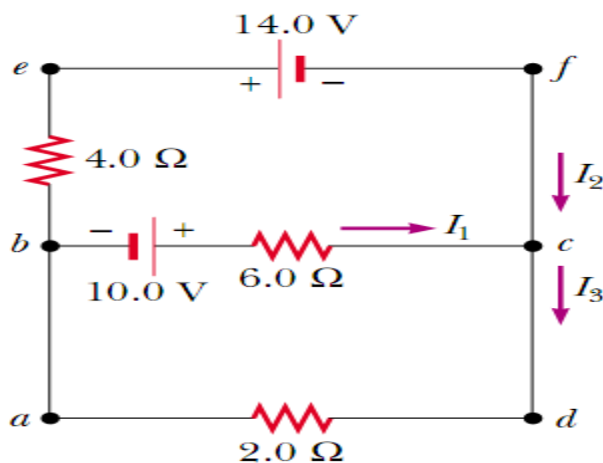- a) Find the currents  $I_1$ ,  $I_2$ , and  $I_3$  in the circuit shown in the figure below. [10mks]



- b) Two resistors connected in series have an equivalent resistance of  $690 \Omega$ . When they are connected in parallel, their equivalent resistance is  $150 \Omega$ . Find the resistance of each resistor. [5mks]
- c) The current in a loop circuit that has a resistance of  $R_1$  is  $2 \text{ A}$ . The current is reduced to  $1.60 \text{ A}$  when an additional resistor  $R_2 = 3 \Omega$  is added in series with  $R_1$ . What is the value of  $R_1$ ? [5mks]

### **QUESTION 5**

- a) State three properties of the magnetic force on a charge moving in a magnetic field  $\mathbf{B}$ . [3mks]
- b) Describe an experiment that demonstrates the magnetic force acting on a current-carrying conductor. Use diagrams to demonstrate your description. [7mks]
- c) Define magnetomotive force (m.m.f.), and state its units. [2mks]
- d) Show that the equation  $s = ut + \frac{1}{2}at^2$  is dimensionally correct. [ 3mks]
- e) A pure inductance of  $120\text{mH}$  is connected in parallel with a  $25\mu\text{F}$  capacitor and the network is connected to a  $100\text{V}$ ,  $50\text{Hz}$  supply. Determine the branch currents [5mks]